

# A 1GHz 133.9fJ Neural Spike Sorting 6-bit Absolute-Value Detector

Jonathan Hurwitz, Vilius Vysniauskas, Nathan Lee

## I. BACKGROUND OF DESIGN

To solve the problem of comparing the absolute value of a 6-bit neural spike input ( $X$ ) to some threshold ( $T$ ), we opted for a custom design using static CMOS and PTL that effectively combines calculating the absolute value and comparison into a single logic stage. Our goal was to output 1 if  $|X| > T$  and 0 otherwise.

In order to avoid creating an adder (to add 1 after flipping bits in the case of a negative input) and then a comparator, we took advantage of the conditions on input:  $X$  will range from -31 to 31 and  $T$  is guaranteed to be positive. If we assume that we have access to the absolute value of  $X$ , then we can figure out whether  $|X| > T$  by using properties of 2's complement and bit-wise addition. By flipping all of the bits of  $T$  and adding to  $|X|$ , we can use knowledge of carries and MSBs to determine the answer. When  $T$ 's bits are flipped, this represents inverting the sign and subtracting 1:  $\bar{T} = -T - 1$ . If we add  $|X|$  to  $\bar{T}$ , the sum will be zero or positive so long as  $|X| > T$ , since  $\bar{T}$  is one less than the negative of  $T$ . The problem has been reduced to determining whether a sum is positive or not.

By inverting  $T$ , we guarantee that the MSB of  $\bar{T}$  will be 1. Assuming  $|X|$  is available, we also know that the MSB of  $|X|$  will be 0. Therefore, the only way to make the sum positive is if the carry-out ( $C_5$ ) of the fifth bit is 1. In this case,  $|X| > T$  and output is 1. If  $C_5$  is 0, then the sum will be negative and  $|X| \leq T$ , with output 0. Our implementation focuses on calculating a 5th bit carry out by using the same logic as a carry lookahead adder would, sans any sum logic. By using CLA logic, we also realized that we could incorporate the absolute-value generator into the carry logic and save an extra adder by setting  $C_{in} = 1$  when  $X$  is negative (sixth bit is 1).

The logical expression for  $C_5$  is:

$$C_5 = G_4 + G_3P_4 + G_2P_4P_3 + G_1P_4P_3P_2 + G_0P_4P_3P_2P_1 + C_{in}P_4P_3P_2P_1P_0 \quad (1)$$

In order to save transistors, this can be factored:

$$C_5 = G_4 + P_4(G_3 + P_3(G_2 + P_2(G_1 + P_1(G_0 + P_0C_{in})))) \quad (2)$$

## II. IMPLEMENTATION

The input stage consists of an input buffer, a MUX to select between  $X$  or  $\bar{X}$ , and an intermediate stage output buffer. The sixth bit of  $X$  is used as the selector for the MUX. If  $X$  is negative,  $\bar{X}$  is selected as input to the second stage. Otherwise,  $X$  is passed directly to an output buffer and then to the second stage. The MSB of  $X$  is also passed into the  $C_{in}$  port of the second stage. Therefore, if  $X$  is negative, the second stage will receive the flipped bits and automatically incorporate addition by 1 via  $C_{in}$ , effectively calculating  $|X|$ . The second stage calculates  $C_5$ .

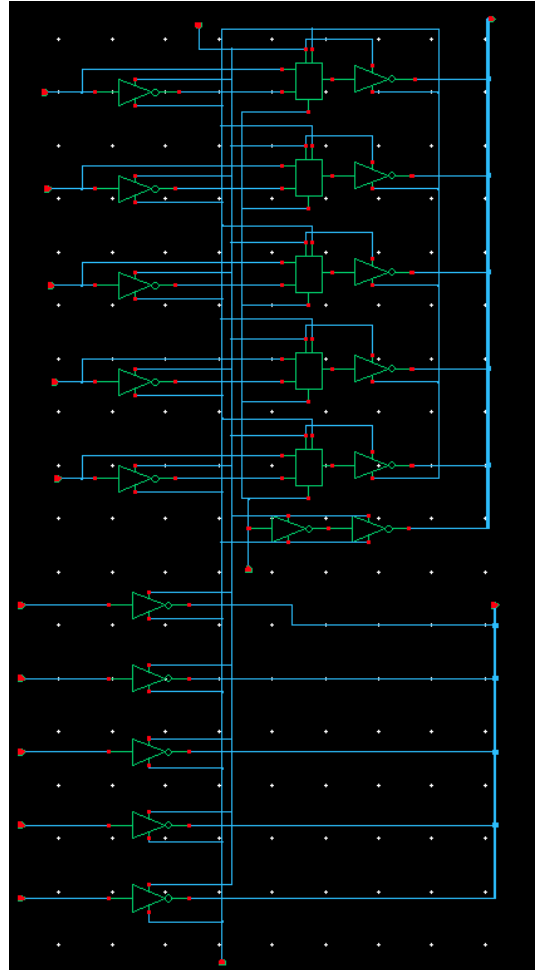


Figure 1: Stage 1 input buffer and MUXes.

The critical path is from  $\bar{X}_0$  input to the output  $C_5$ . This

signal travels through 2 inverters and a T-gate in the first stage, and 9 NOR gates, 2 NAND gates, and 4 inverters in the second stage.

Delay was decreased by reducing the size of fan-out 1 gates to 325:325nm, 325:215nm, 325:215nm for NAND, NOR, and NOT respectively. Since the fan-out of  $C_5$  is 32 reference inverters, we sized the output inverter by 4x to 2.6:1.72um and gradually decreased the driving capability upstream. The  $(n-1)^{th}$  NOR gate was sized at 1.3um:860nm. The  $(n-2)^{th}$  NOR gate was sized at 650:430nm.

### III. LAYOUT

Our layout prioritized minimization of wire lengths. It ended up having an aspect ratio of 1.61. Area minimization was also prioritized, which resulted in a narrow, taller design and hence a larger than expected aspect ratio. When taking into consideration our space savings, area was  $0.631\mu m^2$ . The X limit was 21.905nm and the Y limit was 35.48nm.

The layout has indentations which reduce the total area, but since aspect ratio is calculated based on the limits of X and Y, this does not improve our ratio.

 


Figure 2: Layout cell showing stage 1 integrated with stage 2. The critical path is also shown traced in gray. The yellow boxes outline some of the logical sub-cells.

The critical path is from  $X_0$  input through the carry logic and to the output. This signal goes through the most gates. For reference, the carry logic path can be seen in figure 7 on the last page. It can be represented as follows:

$$t_{crit} = t_{TGate} + 2 * t_{NAND} + 4 * t_{NOT} + 9 * t_{NOR} \quad (3)$$

It was expected that NOR gates would contribute the most to delay on a unit-level.

### IV. SIMULATION RESULTS

The circuit is functionally correct. Results of the testbench simulation are shown below, with  $V_{dd} = 1v$ .

 


Figure 3: Functional check confirming that output is as expected. This was run at  $V_{dd} = 1v$ .

This minimal design allowed us to scale  $V_{dd}$  to  $587.5mV$  without exceeding the limit of the clock period. Energy was  $133.946fJ$ . The worst case  $t_p = 994.267ps$  was within the limit of the clock period (1ns) and was through the critical path. This is shown in Figure 3.

It's possible to maintain low energy usage while leaving enough headroom to compensate for any timing issues. Practically speaking, this is the case that this circuit might operate in when inserted between clocked modules. At  $V_{dd} = 612.5mV$ , there is approximately 106ps of headroom, with a critical path delay  $t_p = 893.999ps$ . This case is shown in Figure 4.

The best-case delay occurs at the worst-case energy usage point, when  $V_{dd} = 1v$ . Energy was  $396.79fJ$  and critical path delay was  $t_p = 370.679ps$ . This is shown in figure 5.

Design Variables		Analyses		
Name	Value	Type	Enable	Arguments
1 VDD	587.5m	tran	<input checked="" type="checkbox"/>	0 90.1n moderate
2 VEXT	1	dc	<input checked="" type="checkbox"/>	t

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 X0		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2 X1		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3 X2		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4 X3		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5 X4		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
6 X5		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
7 OUT		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
8 V0/MINUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
9 V0/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
10 tplh_X0_OUT	956.894p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
11 tphl_X0_OUT	1.03164n	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
12 tplh_X1_OUT	820.848p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
13 tphl_X1_OUT	898.184p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
14 tplh_X2_OUT	689.103p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
15 tphl_X2_OUT	767.414p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
16 tplh_X3_OUT	559.081p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
17 tphl_X3_OUT	636.611p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
18 tplh_X4_OUT	399.268p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
19 tphl_X4_OUT	408.368p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
20 tplh_X5_OUT	416.635p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
21 tphl_X5_OUT	735.101p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
22 Delay_X5_OUT	575.868p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
23 Delay_X4_OUT	403.818p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
24 Delay_X3_OUT	597.846p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
25 Delay_X2_OUT	728.258p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
26 Delay_X1_OUT	859.516p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
27 Delay_X0_OUT	994.267p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
28 Energy	133.946f	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Figure 4: Test bench result with  $V_{dd} = 587.5mV$ . This represents the best-case energy and worst-case delay since it approaches the 1ns limit.

Design Variables		Analyses		
Name	Value	Type	Enable	Arguments
1 VDD	1	tran	<input checked="" type="checkbox"/>	0 90.1n moderate
2 VEXT	1	dc	<input checked="" type="checkbox"/>	t

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 X0		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2 X1		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3 X2		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4 X3		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5 X4		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
6 X5		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
7 OUT		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
8 V0/MINUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
9 V0/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
10 tplh_X0_OUT	372.928p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
11 tphl_X0_OUT	368.429p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
12 tplh_X1_OUT	326.149p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
13 tphl_X1_OUT	335.413p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
14 tplh_X2_OUT	277.825p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
15 tphl_X2_OUT	287.004p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
16 tplh_X3_OUT	229.545p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
17 tphl_X3_OUT	238.615p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
18 tplh_X4_OUT	171.748p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
19 tphl_X4_OUT	164.051p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
20 tplh_X5_OUT	177.662p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
21 tphl_X5_OUT	259.418p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
22 Delay_X5_OUT	218.54p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
23 Delay_X4_OUT	167.899p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
24 Delay_X3_OUT	234.08p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
25 Delay_X2_OUT	282.414p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
26 Delay_X1_OUT	330.781p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
27 Delay_X0_OUT	370.679p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
28 Energy	396.79f	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Figure 6: Test bench result with  $V_{dd} = 1V$ . This is the best-case delay and worst-case energy.

Design Variables		Analyses		
Name	Value	Type	Enable	Arguments
1 VDD	612.5m	tran	<input checked="" type="checkbox"/>	0 90.1n moderate
2 VEXT	1	dc	<input checked="" type="checkbox"/>	t

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 X0		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2 X1		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3 X2		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4 X3		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5 X4		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
6 X5		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
7 OUT		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
8 V0/MINUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
9 V0/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
10 tplh_X0_OUT	860.302p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
11 tphl_X0_OUT	927.696p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
12 tplh_X1_OUT	742.179p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
13 tphl_X1_OUT	810.098p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
14 tplh_X2_OUT	623.813p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
15 tphl_X2_OUT	692.428p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
16 tplh_X3_OUT	506.659p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
17 tphl_X3_OUT	574.755p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
18 tplh_X4_OUT	363.278p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
19 tphl_X4_OUT	371.351p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
20 tplh_X5_OUT	380.279p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
21 tphl_X5_OUT	660.233p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
22 Delay_X5_OUT	520.256p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
23 Delay_X4_OUT	367.314p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
24 Delay_X3_OUT	540.707p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
25 Delay_X2_OUT	658.12p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
26 Delay_X1_OUT	776.139p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
27 Delay_X0_OUT	893.999p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
28 Energy	145.414f	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Figure 5: Test bench result with  $V_{dd} = 612.5mV$ . This is a headroom case.

Carry logic shown below. Stage 1 is represented as black box in the upper left corner.

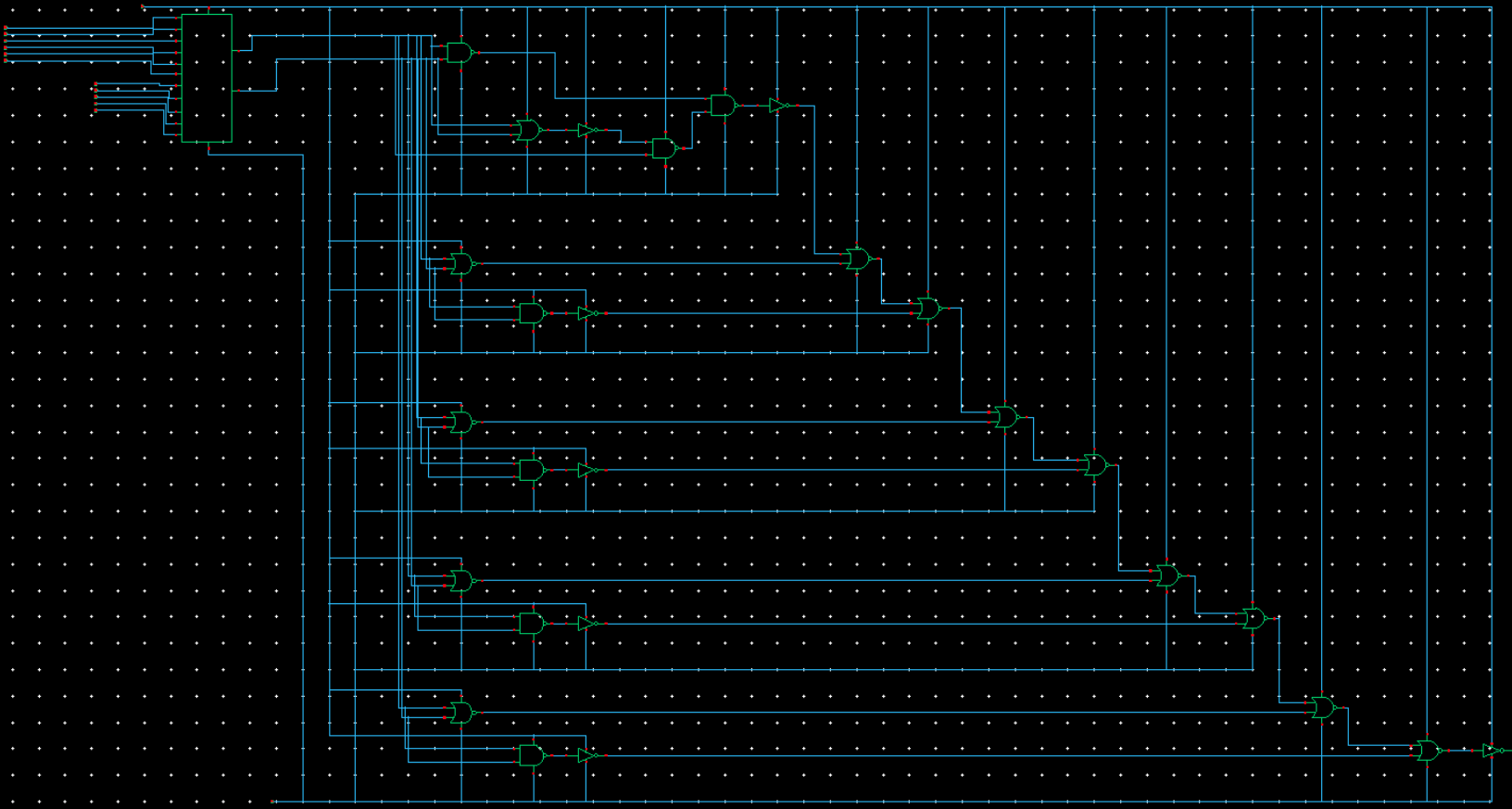


Figure 7:  $C_5$  logic calculation. Stage 1 is shown as a black box on the upper left.